 


Practice 5


- PE implementation & BRAM modeling

Computing Memory Architecture Lab.

Final Project Overview: Matrix Multiplication IP



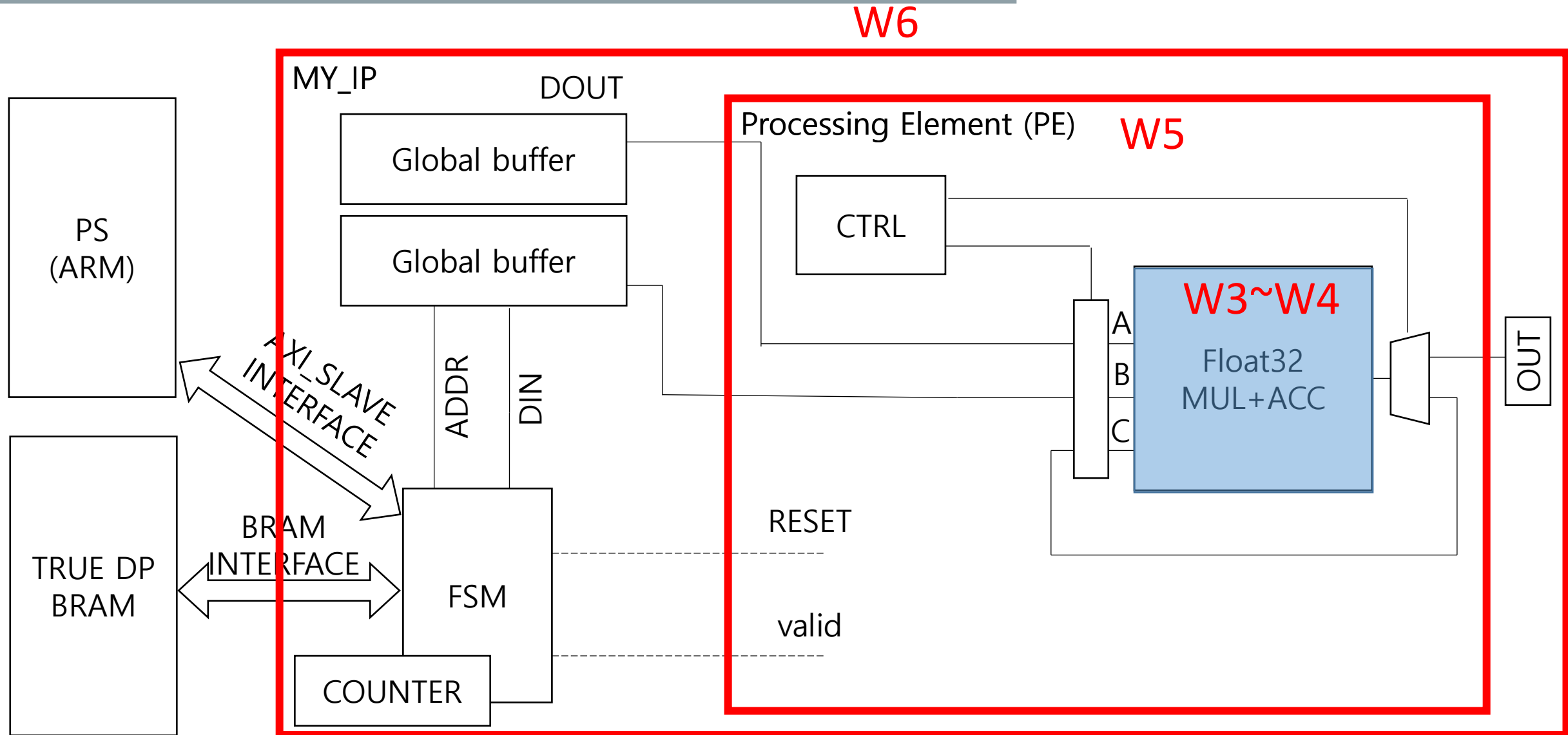Final Project Overview: Matrix Multiplication IP




Final Project Overview: Matrix Multiplication IP

- CNN is our application
 - Convolution layer becomes a matrix-matrix multiplication after convolution lowering
e.g., 32×64 matrix * 64×64 matrix \rightarrow 32×64 matrix
- ARM CPU runs the main function which calls your MM IP on PL
 - MM for 32×64 weight matrix * 64×64 input matrix multiplication
- BRAM is used for data transfer between SW and HW

MM function on Hardware (Software running on CPU)
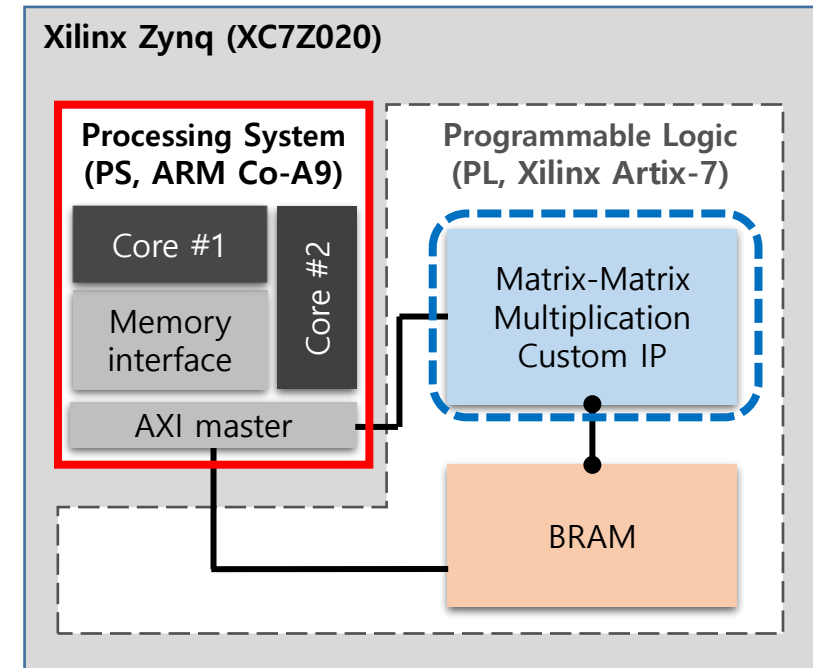
```
for(i=0; i<32; i+=1) {  
  for(j=0; j<64; j+=1) {  
    for(k = 0; k < 64; k++){  
      Output[i][j] += Input[i][k]*W[k][j] Fused multiply  
    }  
  }  
}
```



Main Practice

Practice


1. Implementing BRAM model

- Implement BRAM model & test-bench according to scenarios below.
 - BRAM costs 1 cycle for write and 2 cycles for read.
 - (i.e., BRAM returns value one cycle after it reads address)
(= return the data value one cycle after the BRAM recognizes the changed address.)
- Scenario
 - ① **Make test-bench that instantiates two BRAMs and initialize one BRAM to store its address as data.**
 - (i.e., 'mem[0]' stores '0' and 'mem[1]' stores '1')
 - ② **Then, copy every data from the initialized BRAM to the other BRAM.**
 - Use I/O functions of verilog (e.g., '\$readmemh' and '\$writememh') & text-file (e.g., .txt) to initialize original BRAM and extract values from copied BRAM (access <http://sunshowers.tistory.com/10> to get more information about I/O functions of Verilog).

BRAM SIMULATION

■ BRAM1 -> BRAM2 operation

1. Read start(1.0)

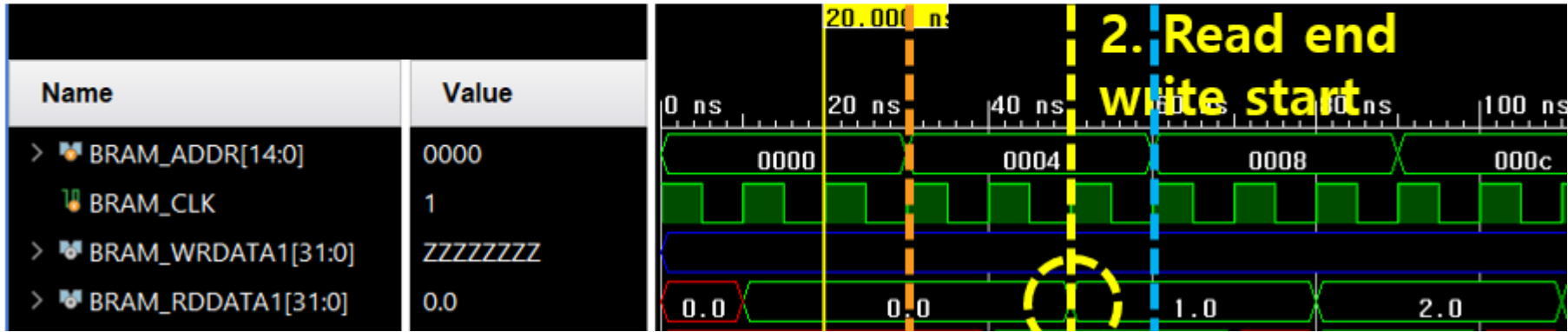

- On the waveform, it also take one cycle until BRAM reads address since we assign it,
- So it takes in total two cycles to return value.

Path of File(input.txt, output.txt)

lab5_ta_txtcheck > lab5_ta_txtcheck.sim > sim_1 > behav > xsim

이름	수정한 날짜	유형	크기
.Xil	2021-03-22 오후 6...	파일 폴더	
xsim.dir	2021-03-22 오후 6...	파일 폴더	
compile	2021-03-22 오후 6...	Windows 배치 파일	1KB
compile	2021-03-22 오후 6...	텍스트 문서	1KB
elaborate	2021-03-22 오후 6...	Windows 배치 파일	1KB
elaborate	2021-03-22 오후 6...	텍스트 문서	1KB
gbl.v	2018-12-07 오후 1...	V 파일	2KB
input	2020-04-11 오전 1...	텍스트 문서	44KB
mkfolder.tcl	2021-03-22 오후 6...	TCL 파일	1KB
mkfolder_behav	2021-03-22 오후 6...	Vivado Waveform...	0KB
mkfolder_vlog.prj	2021-03-22 오후 6...	PRJ 파일	1KB
output	2021-03-22 오후 7...	텍스트 문서	80KB
simulate	2021-03-22 오후 6...	Windows 배치 파일	1KB
simulate	2021-03-22 오후 6...	텍스트 문서	0KB
webtalk.jou	2021-03-22 오후 6...	JOU 파일	1KB
webtalk	2021-03-22 오후 6...	텍스트 문서	1KB
webtalk_23200.backup.jou	2021-03-22 오후 6...	JOU 파일	1KB
webtalk_23200.backup	2021-03-22 오후 6...	텍스트 문서	1KB
xelab.pb	2021-03-22 오후 6...	PB 파일	2KB
xsim	2021-03-22 오후 6...	구성 설정	1KB
xvlog	2021-03-22 오후 6...	텍스트 문서	1KB
xvlog.pb	2021-03-22 오후 6...	PB 파일	1KB


- Make empty simulation file, and Run simulation to make folder.

- From the Project folder, put your input.txt into

<project_name>/<project_name>.sim/sim_1/behav/xsim/input.txt

Practice

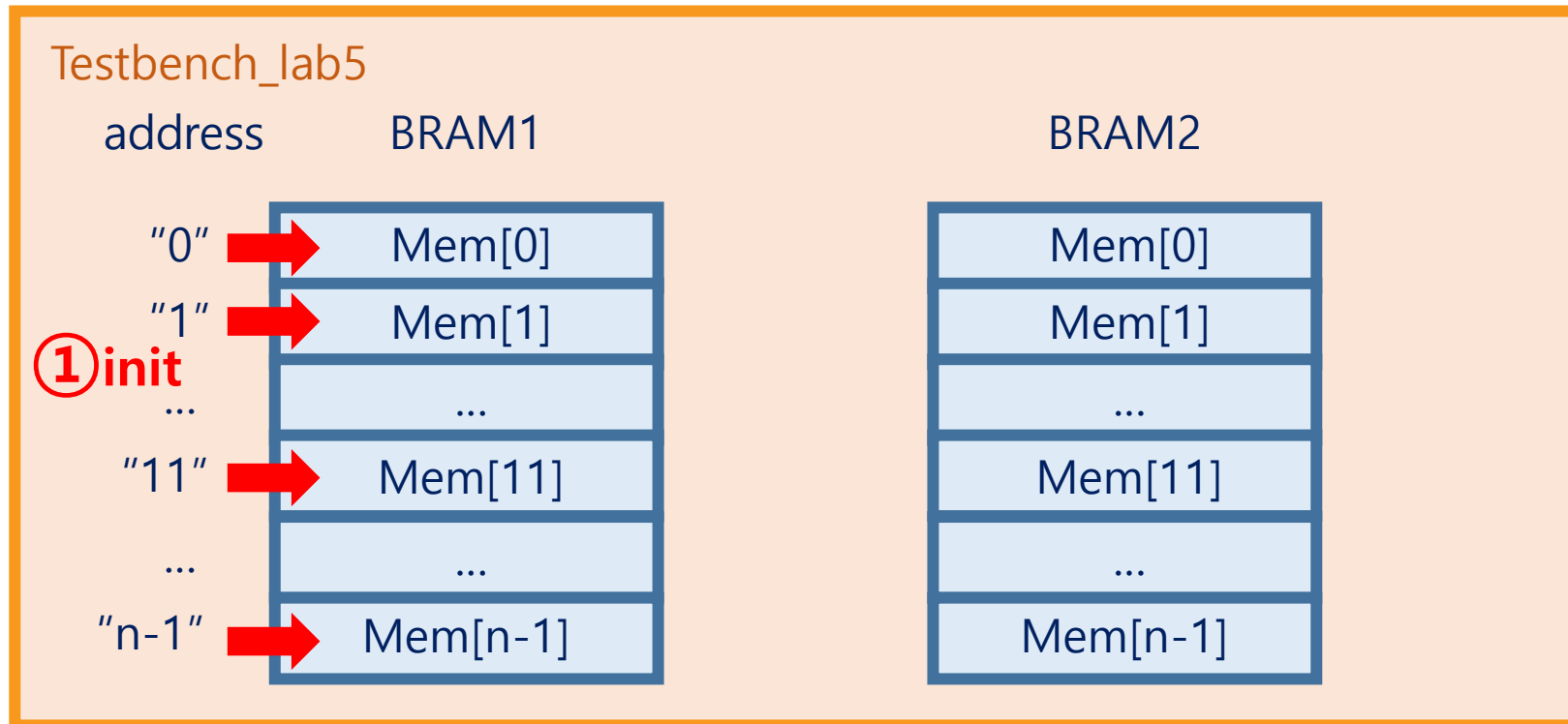
- ① Make test-bench that instantiates two BRAMs and initialize one BRAM to store its address as data.
- (i.e., 'mem[0]' stores '0' and 'mem[1]' stores '1')
 - Add source -> input.txt



Practice

② Then, copy every data from the initialized BRAM to the other BRAM.

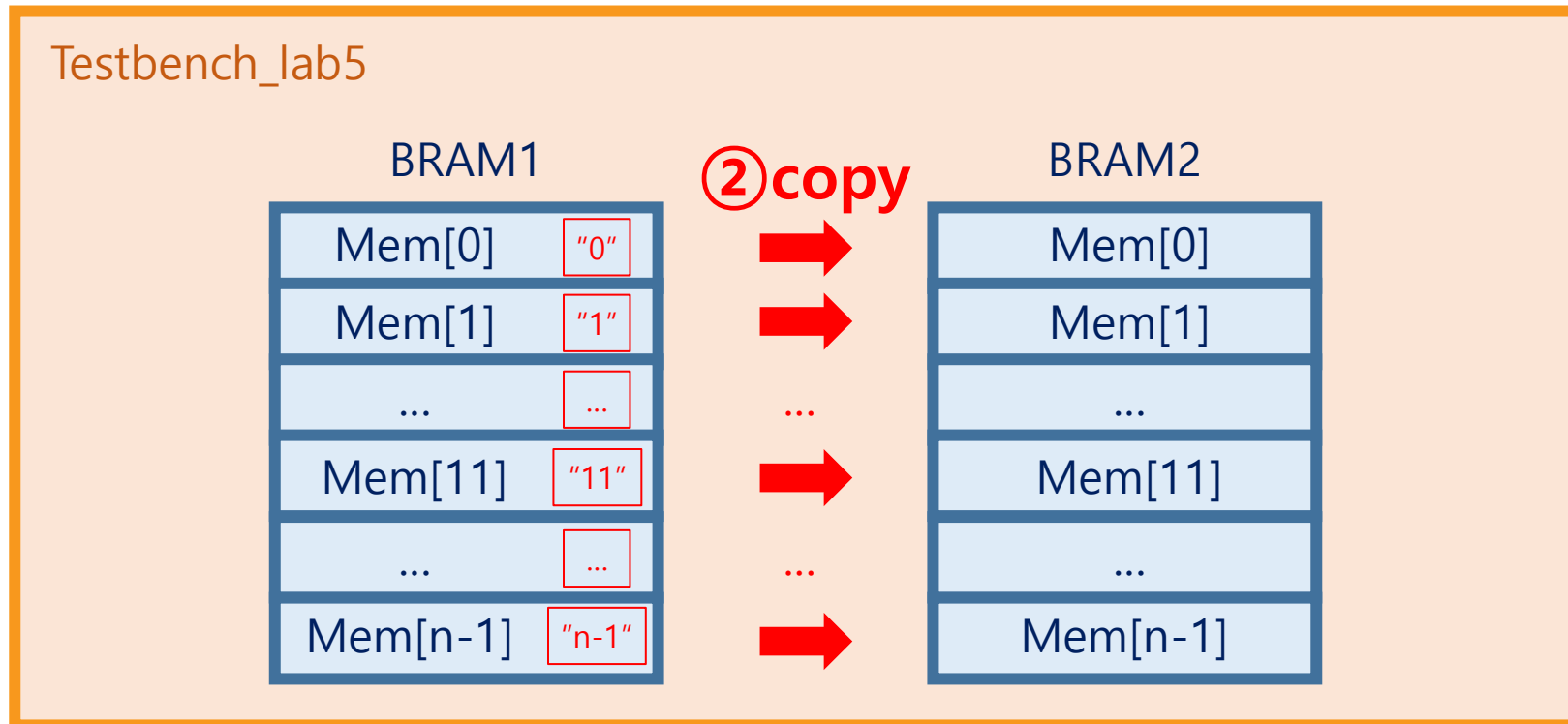- Use I/O functions of verilog (e.g., '\$readmemh' and '\$writememh') & text-file (e.g., .txt) to initialize original BRAM and extract values from copied BRAM




Practice

2. Implementing PE with floating-point fused multiply-adder

- Implement Processing Element (PE) & test-bench according to scenarios below.
- Processing Element (PE) consists of floating-point fused multiply-adder constructed with IP catalog (i.e., you implemented last week).
- Scenario
 - ① There are two global buffer outside of PE, and each memory stores 16 data which is already defined with consecutive addressed (you can set it in TestBench)
 - ② Then, PE gets 16 new data from register outside (test-bench) serially to perform MAC (Multiply-Accumulate) operations with the data stored in local register.
 - Fused multiply-add: $result = (a_{in} * b_{in}) + c_{in}$
 - MAC (Multiply-Accumulate): $result = (a_{in} * b_{in}) + result$
 - ③ Check 16 MAC results in testbench.
 - Note that one MAC operation costs several cycles to compute result and it sets valid bit (i.e. dvalid) high when it finishes each operations.

PE schematic

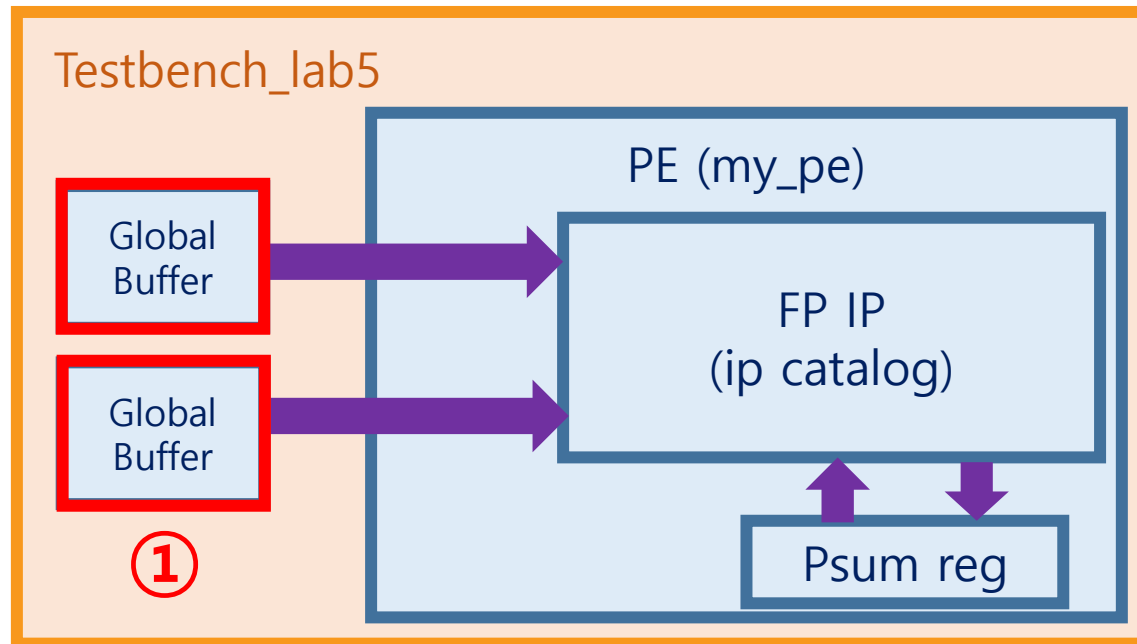
- ① There are two global buffers outside of PE, and each global buffer stores 16 data which is already defined with consecutive addressed (you can set it in TestBench)



$$\text{psum} \leq \text{psum} + \text{ain} * \text{bin}$$

PE schematic


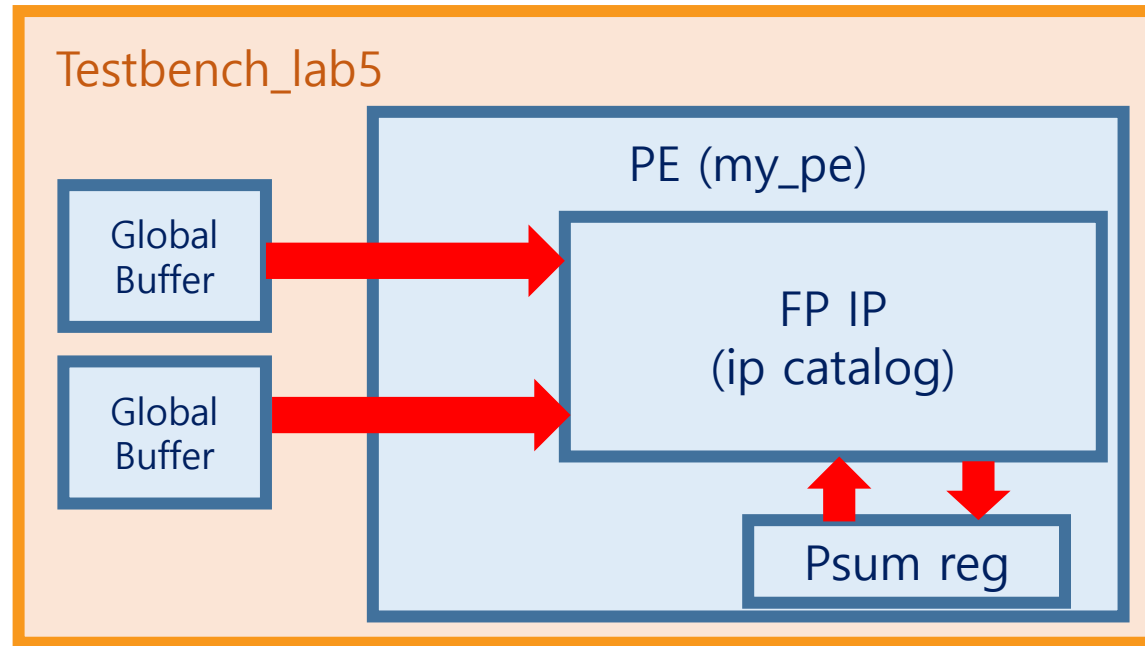
- ② Then, PE gets each 16 data from global buffer outside serially to perform MAC operations with the data stored in local register.
- MAC (Multiply-Accumulate): $result = (a_{in} * b_{in}) + result$




PE schematic

③ Check 16 MAC results.

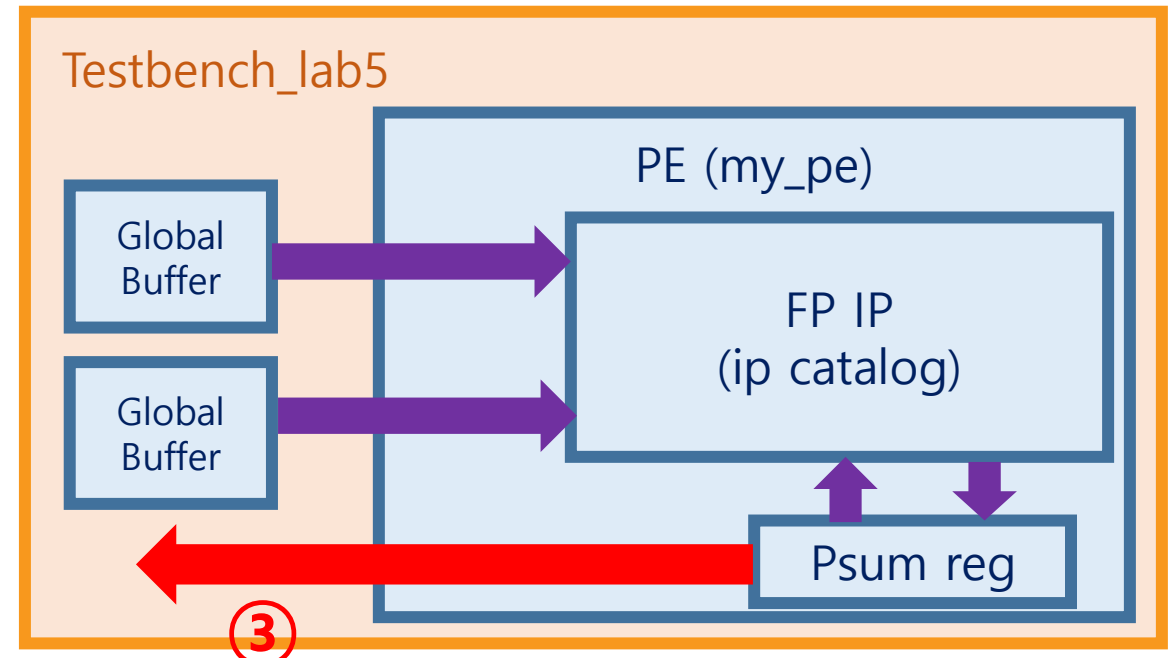 - Note that one MAC operation costs several cycles to compute result and it sets valid bit (i.e. dvalid) high when it finishes each operations.



 Final Project Overview: Matrix Multiplication IP



BRAM Model

```
module my_bram # (  
    parameter integer BRAM_ADDR_WIDTH = 15, // 4x8192  
    parameter INIT_FILE = "input.txt",  
    parameter OUT_FILE = "output.txt"  
)(  
    input wire [BRAM_ADDR_WIDTH-1:0] BRAM_ADDR,  
    input wire BRAM_CLK,  
    input wire [31:0] BRAM_WRDATA,  
    output reg [31:0] BRAM_RDDATA,  
    input wire BRAM_EN,  
    input wire BRAM_RST,  
    input wire [3:0] BRAM_WE,  
    input wire done  
);  
    reg [31:0] mem[0:8191];  
    wire [BRAM_ADDR_WIDTH-3:0] addr = BRAM_ADDR[BRAM_ADDR_WIDTH-1:2];  
    reg [31:0] dout;  
  
    // code for reading & writing  
    initial begin  
        if (INIT_FILE != "") begin  
            // read data from INIT_FILE and store them into mem  
            ...  
        end  
        wait (done)  
        // write data stored in mem into OUT_FILE  
        ...  
    end  
  
    //code for BRAM implementation  
    ...  
endmodule
```

■ Memory configuration

- **Bit width of data:** 32 bits (4 bytes)
- **Bit width of address:** 15 bits
- **# of memory entries:** 8192 ($= 2^{13}$)
- Each external address of which size is 15 bits (i.e., **BRAM_ADDR**) is associated with 1 byte of data. Last two bits are masked and assigned to internal address of which size is 13 bits (i.e., **addr**). It is associated with each entry of **mem** (i.e. it is associated with 4 bytes of data).

■ **BRAM_ADDR:** external address

■ **BRAM_CLK:** clock signal

■ **BRAM_WRDATA:** Data input port of BRAM.

■ **BRAM_RDDATA:** Data output port of BRAM.

■ **BRAM_EN:**

- (**BRAM_EN**==1): **BRAM enabled. BRAM is available for read or write operation.**
- If all of **BRAM_WE** is equal to 0 and **BRAM_EN** == 1, read **mem[addr]** into **BRAM_RDDATA**

■ **BRAM_WE:**

- (**BRAM_WE**[i]==1): **BRAM_WRDATA**[8*(i+1)-1:8*i] is stored into **mem[addr]**[8*(i+1)-1:8*i].

■ **BRAM_RST:** ==1, **BRAM_RDDATA** prints 0

■ **done:** ==1, write data stored in mem into "**OUT_FILE**"

Processing Element (PE)

```
module my_pe #(
    parameter L_RAM_SIZE = 6
)
(
    // clk/reset
    input aclk,
    input aresetn,
    // port A
    input [31:0] ain,
    // port B
    input [31:0] bin,
    // integrated valid signal
    input valid
    // computation result
    output dvalid,
    output [31:0] dout
);

...

endmodule
```

- **aclk:** clock signal
- **aresetn:** negative reset; ==0, reset is activated;
Do not forget to reset in first time in testbench.
- **ain:** input ports connected to MAC
- **bin:** input ports connected to MAC
- **valid:** ==1, MAC gets inputs from its input ports and starts computation; It is divided into three valid signals and assigned to MAC (i.e., it is assigned to **s_axis_a_tvalid**, **s_axis_b_tvalid** and **s_axis_c_tvalid**).
- **dvalid:**
 - ==1, result data from MAC is valid;
 - ==0, result data from MAC is not valid; It is assigned to result valid signal of MAC (i.e., **m_axis_result_tvalid**).
- **dout:** if(dvalid==1), it prints result data from MAC; otherwise it prints 0.

Processing Element (PE) Testbench

```
module tb_my_pe #(
    parameter L_RAM_SIZE = 6
)

    // global buffer
    reg [31:0] gb1 [0:2**L_RAM_SIZE - 1];
    reg [31:0] gb2 [0:2**L_RAM_SIZE - 1];

    initial begin
        ...
    end

    ...

endmodule
```

Homework

- Requirements

- Result

- Attach your project folder with all your verilog codes (e.g., BRAM, PE, test bench)
 - Attach your BRAM waveform(simulation result) with [student_number, name]
 - Test the scenario in slide6.
 - The correct waveform should be shown to confirm the operation of your code.
 - Refer to Practice3 about screenshot.
 - Attach your PE waveform(simulation result) with [student_number, name]
 - Test the scenario in slide9.
 - The correct waveform should be shown to confirm the operation of your code.
 - Refer to Practice3 about screenshot.

- Report

- Explain operation of BRAM with waveform that you implemented
 - Explain operation of PE with waveform that you implemented
 - In your own words
 - Either in Korean or in English
 - # of pages does not matter
 - **PDF only!!**

- **Result + Report to one .zip file**

- Upload (.zip) file on ETL

- Submit one (.zip) file

- zip file name : [Lab05]name1_name2.zip (ex : [Lab05] 홍길동 홍동길 .zip --> **All Team members' name should be included**)

- Due: 4/7(WED) 23:59, Start Early!

- **No Late Submission**